# A Comparison of Asynchronous and Synchronous Digital Design

Sohum Datta


EE241B: Advanced Digital IC


Spring 2017 Project Presentation

# Summary of the two paradigms

SYNCHRONOUS	ASYNCHRONOUS	
+ easier to design and verify	- harder to synthesize, verify and P&R (not many tools ⊗ )	
+ easy robustness guarantees (setup &hold only)	- special handshake (eg. 4- phase) to guard against glitch	
- Clock fidelity limit to scalability	+ automatic ordering, inherently scalable	
- Slack (and power) lost in most paths	+ Timing close to slack-free; power efficient (asymptotically)	
<ul> <li>moore's law ending → parallel modules (different clk domains)</li> <li>→ interface synchronization</li> </ul>	+ seamless integration of asynchronous modules	
 
# Basic Gate: Muller "Completion" Element




 

(Synthesized using *Petrify* tool from Signal Transition Graph specification)


Α	В	Out	
1	1	1	
1	0	No Change	
0	1	No Change	
0	0	0	

## Basic building blocks

 


(the Muller pipeline for local "clock" generation)

# The 3-stage Asynchronous pipeline

 


#### The Virtex-5 IODELAY Primitive

 


- The Parameter  $IDELAY\_VALUE$  is number of delay taps (0 63). Tap delay resolution is 31 ps. at config. freq. of 50 MHz.
- Path delay can be as high as 3.83 ns (3 IODELAYS). Placement (hence delay) depends on number of IODELAYs in the design.

 
#### Delay Optimization on Xilinx Virtex 5 FPGA



#### After P&R on Xilinx Virtex-5

 


(asynchronous design)

 


(synchronous design)

#### After P&R on Xilinx Virtex-5

 

(asynchronous design)

 

(synchronous design)

## Results of Comparison

Resource Summary	SYNC	ASYNC	Change
SLICE Regs.	1413	1446	+33 (23 %)
SLICE LUTs	2358	2395	+37 (16%)
BUFG/ BUFGCTRL	2	5	+ 3
mmult Throughput	67.4 MIPS	24.1 MIPS	-43.3 MIPS (-64%)

• Throughput reduction as the Muller pipeline is **alternating HIGH and LOW** (about half throughput lost). The rest due to routing and IODELAY overestimates.

#### **Conclusion and Comments**

- A **lot of time** was spent optimizing the DELAY variables. These circuits usually require asynchronous primitives **directly on the FPGA board** (eg. Montage)
- The ML505 Development board **does not have supply resistors** to measure runtime power.
  - Due to lack of resources, I could not move to another board for power measurements.
  - Could have sourced a voltage regulator externally from a breadboard.
- An ASIC tool chain would be a fairer comparison. Using 2 Latches (hence, SLICES) for 1 Muller C gate is very wasteful. Some tools exists (eg. Balsa, Petrify, ...) but are hard to setup and time-consuming.
- Have a working asynchronous pipeline! Project challenges indicative why asynchronous **not yet economic**.

# Thank you